

## Week 15

Logic Gates

Fall 2013

## Student Responsibilities — Week 15

- ▶ **Reading:** Textbook, Section 11.1 – 11.3
- ▶ **Attendance:** Finally! Encouraged

### Week 15 Overview

How Boolean logic and Boolean algebra relate to computer circuits and chips.

- ▶ Sec 11.1 Boolean Functions
- ▶ Sec 11.2 Representing Boolean Functions
- ▶ Sec 11.3 Logic Gates

## 9.1 Boolean Functions

**Boolean Algebra** provides the operations [*complement, product, sum*] and rules for working with the set  $\{0, 1\}$ .

**Complement** (denoted with bar):  $\bar{0} = 1, \bar{1} = 0$ .

**Product** (denoted with AND,  $\bullet$ , or implicit):

$$1 \bullet 1 = 1 \quad 1 \bullet 0 = 0 \quad 0 \bullet 1 = 0 \quad 0 \bullet 0 = 0$$

**Sum** (denoted with OR or +):

$$1 + 1 = 1 \quad 1 + 0 = 1 \quad 0 + 1 = 1 \quad 0 + 0 = 0$$

**Precedence of Operators:** complement, product, sum

**Example:**  $(1 + 0) \bullet \overline{(0 \bullet 1)} = 1 \bullet \bar{0} = 1 \bullet 1 = 1$

## Boolean Functions

Let  $B = \{0, 1\}$

- ▶ A **Boolean variable**  $x$  assumes values only from  $B$ .
- ▶ A **Boolean Function of Degree  $n$**  is a function from  $B^n$ , the set  $\{(x_1, x_2, \dots, x_n) | x_i \in B, 1 \leq i \leq n\}$ , to  $B$ .  
Function values are often displayed in tables.

## Boolean Expressions

- ▶ **Boolean Expressions**, which can represent Boolean functions, are made up from Boolean variables and operations.
- ▶ They are defined recursively as follows:
  - ▶  $0, 1, x_1, x_2, \dots, x_n$  are Boolean expressions.
  - ▶ If  $E_1$  and  $E_2$  are Boolean expressions, then so are their complements, their product, and their sum:  
 $\bar{E}_1, (E_1 E_2),$  and  $(E_1 + E_2)$
- ▶ Each Boolean expression represents a Boolean function.

## Function Evaluation

To evaluate a function, we substitute 0's and 1's for the variables in the same way we did for Truth Tables.

$x$	$y$	$z$	$\bar{x}$	$yz$	$F(x, y, z) = \bar{x} + yz$
1	1	1	0	1	1
1	1	0	0	0	0
1	0	1	0	0	0
1	0	0	0	0	0
0	1	1	1	1	1
0	1	0	1	0	1
0	0	1	1	0	1
0	0	0	1	0	1

### Equivalence of Boolean Functions

Two Boolean functions  $F$  and  $G$  are **equivalent** if and only if when they are evaluated on the variables  $b_1, b_2, \dots, b_n \in B$ :

$$F(b_1, b_2, \dots, b_n) = G(b_1, b_2, \dots, b_n)$$

All these functions are equivalent:  $xy \quad xy + 0 \quad xy \bullet 1$

### Boolean Operators on Functions

- ▶ The **complement** of the Boolean function  $F$  is the function  $\bar{F}$ , where:

$$\bar{F}(x_1, \dots, x_n) = \overline{F(x_1, \dots, x_n)}$$

- ▶ The **Boolean sum**  $F + G$  is defined by:

$$(F + G)(x_1, \dots, x_n) = F(x_1, \dots, x_n) + G(x_1, \dots, x_n)$$

- ▶ The **Boolean product**  $FG$  is defined by:

$$(FG)(x_1, \dots, x_n) = F(x_1, \dots, x_n)G(x_1, \dots, x_n)$$

### Degree of a Function

The **degree** of a Boolean function is the number of different variables upon which it depends.

$F(x_1, \dots, x_n)$  has degree  $n$ .

x	y	$F_1$	$F_2$	$F_3$	$F_4$	$F_5$	$F_6$	$F_7$	$F_8$
1	1	1	1	1	1	1	1	1	1
1	0	1	1	1	1	0	0	0	0
0	1	1	1	0	0	1	1	0	0
0	0	1	0	1	0	1	0	1	0

x	y	$F_9$	$F_{10}$	$F_{11}$	$F_{12}$	$F_{13}$	$F_{14}$	$F_{15}$	$F_{16}$
1	1	0	0	0	0	0	0	0	0
1	0	1	1	1	1	0	0	0	0
0	1	1	1	0	0	1	1	0	0
0	0	1	0	1	0	1	0	1	0

Degree	Number
1	4
2	16
3	256
4	65,536
5	4,294,967,296
6	18,446,744,073,709,551,616

Boolean Function with degree  $n$

There are  $2^n$   $n$ -tuples of 0's and 1's — representing all possible combinations of the  $n$  variable values.

Each function is an assignment of 0's and 1's to each of these  $n$ -tuples

Hence, there are  $2^{2^n}$  different Boolean functions of degree  $n$ .

### Boolean Identities

Identity	Name
$\overline{\bar{x}} = x$	Law of Double Complement
$x + x = x$ $xx = x$	Idempotent Laws
$x + 0 = x$ $x(1) = x$	Identity Laws
$x + 1 = 1$ $x(0) = 0$	Dominance Laws
$x + y = y + x$ $xy = yx$	Commutative Laws
$x + (y + z) = (x + y) + z$ $x(yz) = (xy)z$	Associative Laws
$x + yz = (x + y)(x + z)$ $x(y + z) = xy + xz$	Distributive Laws
$\overline{xy} = \bar{x} + \bar{y}$ $\overline{x + y} = \bar{x}\bar{y}$	De Morgan's Laws

### Boolean Algebra

A **Boolean algebra** is a set  $B$  with:

- ▶ two binary operations,  $\vee$  and  $\wedge$
- ▶ elements 0 and 1
- ▶ a unary operation such that the following properties hold  $\forall x, y, z \in B$ :

$x \vee 0 = x$ $x \wedge 1 = x$	Identity Laws
$x \vee \bar{x} = 1$ $x \wedge \bar{x} = 0$	Dominance Laws
$(x \vee y) \vee z = x \vee (y \vee z)$ $(x \wedge y) \wedge z = x \wedge (y \wedge z)$	Associative Laws
$x \vee y = y \vee x$ $x \wedge y = y \wedge x$	Commutative Laws
$x \vee (y \wedge z) = (x \vee y) \wedge (x \vee z)$ $x \wedge (y \vee z) = (x \wedge y) \vee (x \wedge z)$	Distributive Laws

## Equivalent Collections

Collections which satisfy all three Boolean Algebra properties include:

- ▶  $B = \{0, 1\}$ , with  $\{+, \bullet\}$  and the complement operator
- ▶ The set of propositions in  $n$  variables with the  $\vee$  and  $\wedge$  operators, F and T, and the negation operator.
- ▶ The set of subsets of a universal set  $U$  with  $\cap$  and  $\cup$ ,  $\emptyset$ , and set complementation operator.

## They All Tie Together

To establish results about each of

**Boolean expressions**  
**Propositions**

and

**Sets,**

we need only prove results about abstract Boolean Algebras!

## Section 11.3 — Logic Gates


- ▶ Computer chips are made up of vast numbers of circuits.
- ▶ Circuits can be designed using the rules of Boolean algebra.
- ▶ The basic components of circuits are called gates and each type of gate implements a Boolean operation.
- ▶ We can use the rules of Boolean algebra to combine gates into circuits that perform various tasks. Input and output will both be from the set 0, 1.

- ▶ The **combinatorial circuits** or **gating networks** we'll be studying depend only upon the **inputs**, and not on the **current state** of the circuit - i.e., they have no memory capabilities.
- ▶ The three types of elements we'll use to create circuits are:
  - ▶ the **inverter**, which produces the complement of its input value;
  - ▶ the **OR** gate, which produces the sum of its inputs, and
  - ▶ the **AND** gate, which produces the product of its inputs


## Symbolic Gates

The symbols used for these types of elements are shown below:


- ▶ **inverter:**

 

- ▶ **OR gate:**


 


- ▶ **AND gate:**

 

  
## Multiple Input Gates

- ▶ We can also have multiple input OR and AND gates. Examples of gates with  $n$  inputs are shown below:




- ▶ Inputs enter inverters and gates from their left sides and output is shown leaving from their right sides. There is only one way for current to flow through these components.


- ▶ Combinational circuits can be constructed using a combination of inverters, OR, and AND gates.
- ▶ When combinations of circuits are formed, some gates may share inputs. There are two common ways to show this:
  - ▶ One is to give the same name to the separate inputs for each gate, as shown in the first figure on the next slide.
  - ▶ The other is to use branches that indicate all gates using a given input. This is shown in the second figure.

 

Examples of Circuits:  $(x + y)\bar{x}$

 

 Examples of Circuits:  $\bar{x}(y + \bar{z})$



Two-Switch Light (0 = off, 1 = on)

Flipping either switch should turn the light on if it's off, and off if it's on.

2-switch light		
x	y	F(x, y)
1	1	1
1	0	0
0	1	0
0	0	1

Three-Switch Light (0 = off, 1 = on)

3-switch light			
x	y	z	F(x, y, z)
1	1	1	1
1	1	0	0
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	1
0	0	0	0


### Three Voters with Majority Rule

3-Votes, Majority Rules			
x	y	z	M(x, y, z)
1	1	1	
1	1	0	
1	0	1	
1	0	0	
0	1	1	
0	1	0	
0	0	1	
0	0	0	

### Adders

- ▶ One of the most common uses for a computer is numerical computation.
- ▶ We will next see how we can design circuits to carry out addition.
- ▶ A **half adder** adds two bits without considering any carry from a previous addition.
  - ▶ The **input** will be two values,  $x$  and  $y$ , each either 0 or 1.
  - ▶ The **output** will be the sum bit  $s$ , and the carry bit,  $c$ .
  - ▶ This circuit is called a **multiple output circuit** since it has more than one output.

Half-Adder I/O			
INPUT		OUTPUT	
x	y	s	c
1	1	0	1
1	0	1	0
0	1	1	0
0	0	0	0

 

### Full Adder

- ▶ The **full adder** is used to compute the sum bit and carry bit when two bits and a carry are added.
- ▶ The **inputs** to the full adder are the bits  $x$  and  $y$ , and the carry  $c_i$ .
- ▶ The **outputs** are the sum bit  $s$  and the new carry  $c_{i+1}$ .

Full-Adder I/O				
INPUT			OUTPUT	
x	y	$c_i$	s	$c_{i+1}$
1	1	1	1	1
1	1	0	0	1
1	0	1	0	1
1	0	0	1	0
0	1	1	0	1
0	1	0	1	0
0	0	1	1	0
0	0	0	0	0

This full adder utilizes half adders rather than building them from scratch:

